


Candidate 3 evidence

SECTION 1 — 20 marks

Attempt ALL questions


MARKS
DO NOT WRITE IN THIS MARGIN

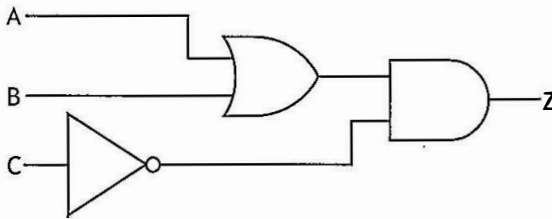1. An electronic engineer requires the following circuit as part of a hand-held product. It is to be made using individual integrated circuits (ICs).



- (a) Draw a NAND equivalent for the circuit shown above.

3

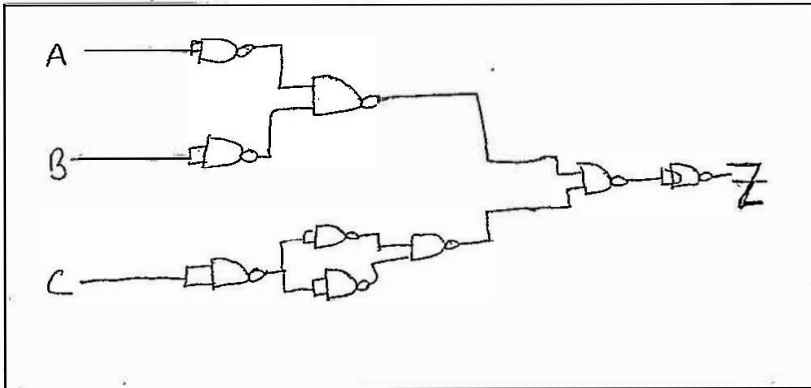


- (b) Explain why the engineer chose to use the NAND equivalent circuit in the product rather than the original circuit.

1


Because it is more efficient

MARKS
DO NOT
WRITE IN
THIS
MARGIN

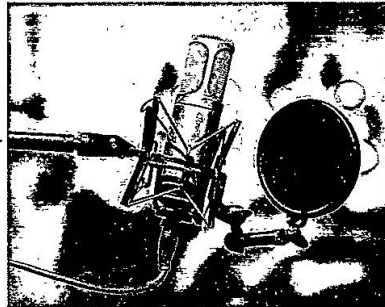2. A microphone in a recording studio produces a maximum output signal of 2.0 mV.



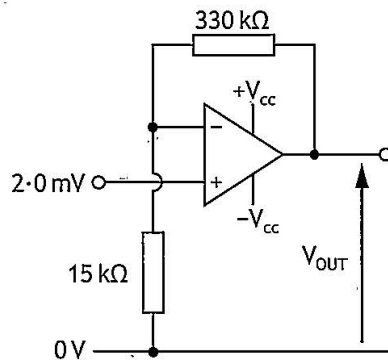The following circuit is used to amplify the signal so that it can be recorded.



- (a) Calculate the output voltage from the op-amp shown above.

1

~~$$V_1 = 2 \times 10^{-3}$$

$$V_2 = ?$$

$$R_1 = 330 \times 10^3$$

$$R_2 = 15 \times 10^3$$~~

~~$$\frac{V_1}{V_2} = \frac{R_2}{R_1}$$

$$\frac{2 \times 10^{-3}}{V_2} = \frac{330 \times 10^3}{15 \times 10^3}$$

$$V_2 = \frac{2 \times 10^{-3} \times 15 \times 10^3}{330 \times 10^3}$$

$$V_2 = 9.09 \times 10^{-5} \text{ V}$$~~

$$\frac{V_1}{V_2} = \frac{R_2}{R_1}$$

$$2 \times 10^{-3} - 0.7$$

$$= 0.698 \text{ V}$$

MARKS	DO NOT WRITE IN THIS MARGIN
1	
1	

2. (continued)

- (b) Describe how the gain of the op-amp circuit could be increased.


make the two resistors equal

The mixing desk in the studio needs to combine the signals from a number of microphones and instruments to produce one output signal for the speakers.

- (c) State the op-amp configuration required to perform this task.

Summing op-amp

3. A frame structure is shown below.

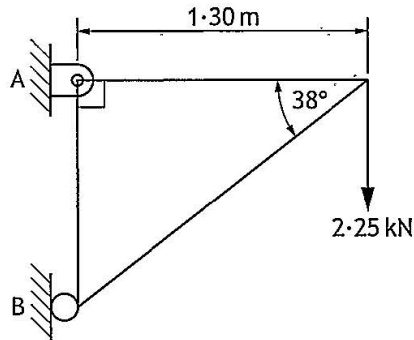

Calculate the magnitude and indicate the direction of the reaction at B.

4

$$90^\circ + 38^\circ = 128^\circ$$

$$180^\circ - 128^\circ = 52^\circ$$

$$2250 \sin 52 + 2250 \cos 52$$

$$= 1773.02 + 1385.2$$

$$= 3158.22 \text{ N}$$

$$\text{magnitude} = 3158.22 \text{ N}$$

$$\text{direction} = 180^\circ + 38^\circ$$

$$= 218^\circ$$

$$\underline{\underline{3158.22 @ 218}}$$

4. An air pressure supply system in a car garage will be operated by programmable control. The system must meet the following specification.
- The system is activated when a user presses a start button
 - The pumping system then switches on
 - The air pressure is monitored by an analogue sensor
 - When the air pressure rises above a set level (100), the pump switches off
 - A light must flash five times to indicate that the air pressure has reached the set level
 - The system then resets, ready for the next user

Input	Pin	Output
	7	Pump
	6	Light
Start button	1	
Pressure sensor	0	

Part of the same test program is shown below in PBASIC and ARDUINO code.

```

let dirs = %11110000
symbol pressure = b4

main: if pin1 = 1 then main
    high 7

check: readadc 0, pressure

if pressure ≤ 200 then check
    low 7

    for b3 = 0 to 5
        high 6
        pause 200
        low 6
        pause 200
    next b3

goto main

```

```

int Pressure = 0;
int Pressuresensor = 0;
int Pump = 7;
int Light = 6;
int Startbutton = 1;

void setup(){
  pinMode (Pressuresensor, INPUT);
  pinMode (Startbutton, INPUT);
  pinMode (Pump, OUTPUT);
  pinMode (Light, OUTPUT);
}

void loop(){
  if (Startbutton == LOW) {
    digitalWrite(Pump, HIGH);
  } else {
    digitalWrite(Pump, LOW);
  }
  Pressure = analogRead (Pressuresensor);
  if (Pressure <= 200){
    digitalWrite (Pump, LOW);
  }
  for(int counter=0; counter<=5;
  counter=counter+1)
  {digitalWrite(Light, HIGH);
  delay(200);
  digitalWrite(Light, LOW);
  delay(200);
  }
}

```

MARKS	DO NOT WRITE IN THIS MARGIN
2	

4. (continued)

There are three faults in the program shown opposite.
Identify the lines where the faults are and write the corrected code.
Complete for **either** PBASIC or ARDUINO.

2

The first fault is shown below.

Correction 1 PBASIC *main: if pin1 = 0 then main*

Correction 1 ARDUINO *if (Startbutton == HIGH) {*

Correction 2

PBASIC *if pressure ≤ 100 then check*


Correction 3

ARDUINO *if (Pressure <= 100) {*

[Turn over

MARKS	DO NOT
	WRITE IN THIS MARGIN

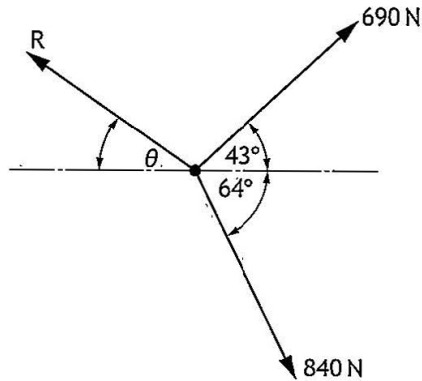5. A concurrent force system is shown below.



Calculate the magnitude and angle of the force R required to maintain equilibrium.

4

$$\begin{aligned}
 \text{magnitude} &= (690 \sin 43 + 690 \cos 43) + (-840 \sin 64 + 840 \cos 64) \\
 &= (470.5 + 504.6) + (-754.9 + 368.23) \\
 &= \underline{\underline{588.43}} \\
 \theta &= \tan^{-1}(588.43) \\
 &= \underline{\underline{89.9^\circ}}
 \end{aligned}$$


MARKS
DO NOT
WRITE IN
THIS
MARGIN

6. The temperature in a room can be set by a signal from a mobile phone or directly using a control panel.

A heating system monitors the temperature of the room and maintains the set temperature.

Complete the control diagram below for the heating of the room.

3

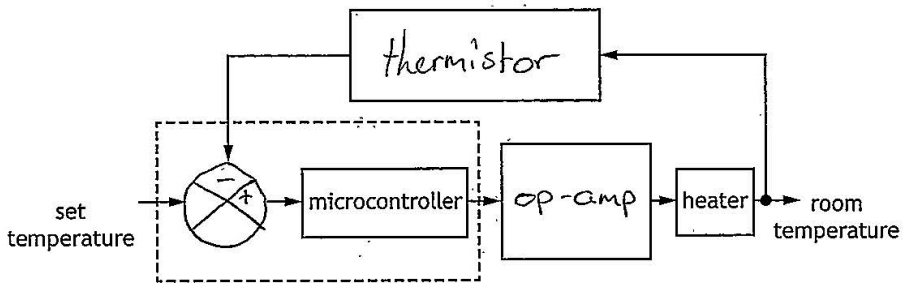

[Turn over


SECTION 2 — 90 marks

Attempt ALL questions

MARKS

DO NOT
WRITE IN
THIS
MARGIN

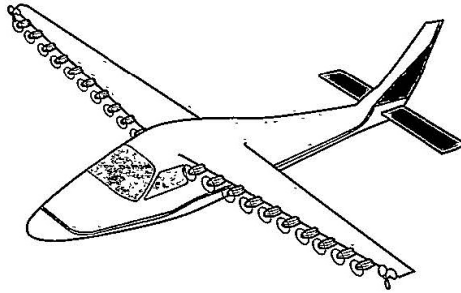7. A prototype of an electrically powered aeroplane is being developed and tested by a team of engineers.



The aeroplane is powered by 22 motor-driven propellers that each supply 18 kW.

- (a) Calculate the rotational speed of each motor if it produces 23 Nm of torque.

1

$$\begin{array}{l}
 P = 18000 \\
 F = 23 \\
 V = ?
 \end{array}
 \left.
 \begin{array}{l}
 P = FV \\
 V = \frac{P}{F} \\
 = \frac{18000}{23} \\
 = \underline{\underline{782.6 \text{ ms}^{-1}}}
 \end{array}
 \right\}$$

When operating at full power the aeroplane is 73% efficient. The aeroplane's battery stores 320 MJ when fully charged.

- (b) Calculate how much time the aeroplane can run at full power before the battery runs out.

2

$$\begin{array}{l}
 P = 18000 \times 22 \\
 = 396 \times 10^3 \\
 E = 320 \times 10^6 \\
 t = ?
 \end{array}
 \left.
 \begin{array}{l}
 P = 396 \times 10^3 \\
 E = 320 \times 10^6 \\
 t = ?
 \end{array}
 \right\}
 \begin{array}{l}
 P = \frac{E}{t} \\
 t = \frac{E}{P} \\
 = \frac{320 \times 10^6}{396 \times 10^3} \\
 = 1.24 \\
 t = \frac{E}{P} \\
 = \frac{320 \times 10^6}{396 \times 10^3} \\
 = \underline{\underline{808.08 \text{ seconds}}}
 \end{array}$$

7. (continued)

MARKS	DO NOT WRITE IN THIS MARGIN
-------	--------------------------------------

Improving efficiency is a key task for the engineers who design the aeroplane.

- (c) Explain one economic and one social impact of improving the efficiency of the aeroplane.

2

Economic less fuel is used meaning less
pollution

Social it is more cost effective for
both passengers and airline company

When the aeroplane lands, the propellers are used to transform its kinetic energy back into electrical energy to recharge the batteries as part of a regenerative braking system.

The combined mass of the aeroplane and passengers is 4800 kg and the regenerative braking system is 64% efficient.

- (d) Calculate the energy recovered if the aeroplane's velocity changes from 95 m s^{-1} to 25 m s^{-1} .

3

$E_k = ?$ $M = 4800$ $v^2 = 70$	$E_k = \frac{1}{2} m v^2$ $= \frac{1}{2} \times 4800 \times 70^2$ $= 11760000 \text{ J}$ $= \underline{\underline{11.76 \text{ MJ}}}$
$v^2 = 95^2 - 25^2$ $= 70 \text{ m s}^{-1}$	

[Turn over

7. (continued)

Bearings are required on the propellers to ensure that they can spin and transfer kinetic energy to make the aeroplane move.

- (e) Explain, giving two reasons, why friction needs to be minimised in the bearings.


2

Friction needs to be minimised because friction can cause the propellers to heat up and get damaged. It also needs to be minimised because the friction will force the motors to work harder making it less efficient.

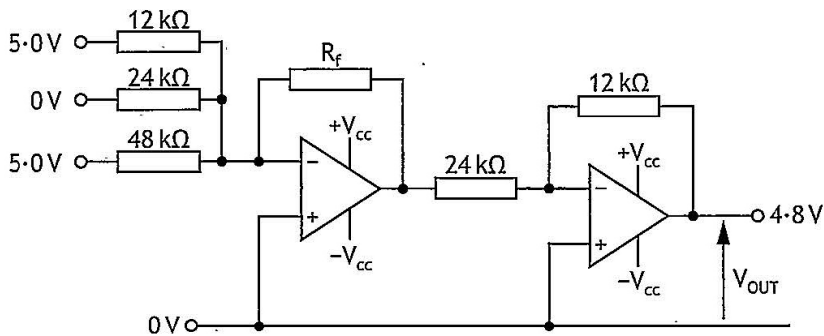7. (continued)

The pilot controls the speed of the aeroplane by moving an accelerator lever. A signal is sent from the lever to a microcontroller which, in turn, sends a signal to an op-amp circuit and the motors' drive systems.

The op-amp circuit is shown below. Each pin from the microcontroller gives a 5.0V signal when on.




- (f) Calculate the value of the feedback resistor, R_f , when V_{OUT} is 4.8V.

3

$$\begin{aligned}
 & \left. \begin{array}{l} V_o = 4.8 \\ R_f = ? \\ R_i = 48000 \\ V_i = 5 \end{array} \right\} \\
 & V_o = -\frac{R_f}{R_i} V_i \\
 & R_f = \frac{V_o R_i}{V_i} \\
 & \quad = \frac{4.8 \times 48000}{5} \\
 & \underline{\underline{R_f = 46.08 \text{ k}\Omega}}
 \end{aligned}$$

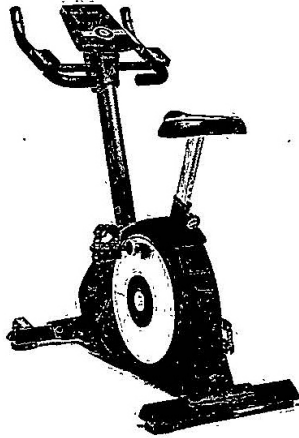8. An exercise bike has an electronic monitoring system to tell users if they are pedalling within a set range of speeds.




A speed sensor produces an output voltage, V_{speed} , in proportion to the speed of the pedals.


If the voltage is below the lower limit, a bank of LEDs lights to say, 'SPEED UP'.

If the voltage is above the higher limit, a second bank of LEDs lights to say, 'TAKE IT EASY'.

The control circuit is shown below.

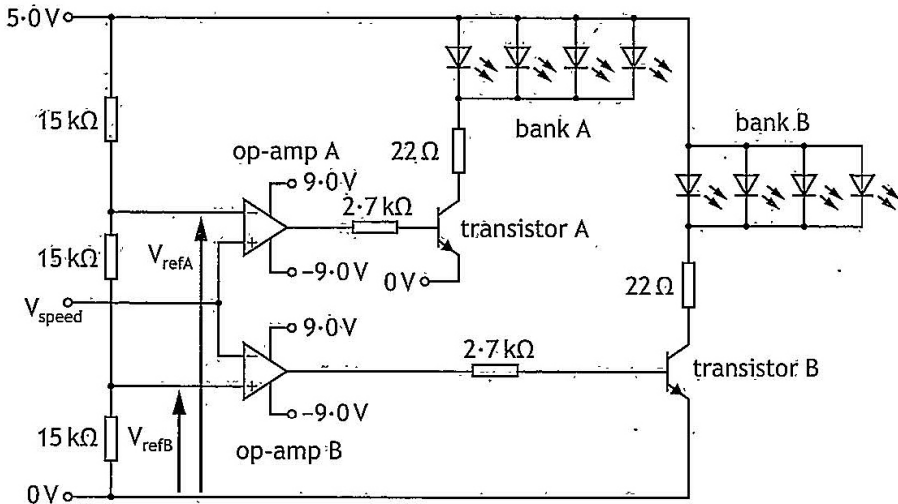

8. (continued)

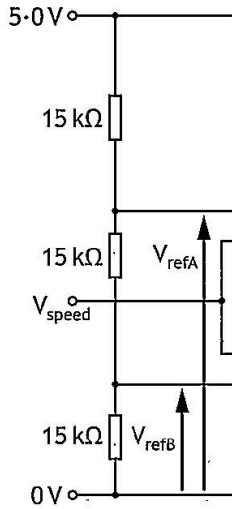

A section of the circuit is shown above.

(a) Calculate the reference voltage V_{refA} .


2

$$\begin{array}{l}
 V_{refA} = ? \\
 V_S = 5 \\
 R_1 = 15000 \\
 R_2 = 15000
 \end{array}
 \left. \vphantom{\begin{array}{l} V_{refA} = ? \\ V_S = 5 \\ R_1 = 15000 \\ R_2 = 15000 \end{array}} \right\}
 \begin{array}{l}
 V_{refA} = \frac{R_2}{R_1 + R_2} \times V_S \\
 = \frac{15000}{30000} \times 5 \\
 = \underline{\underline{2.5V}}
 \end{array}$$

[Turn over

8. (continued)

A section of the circuit is shown.

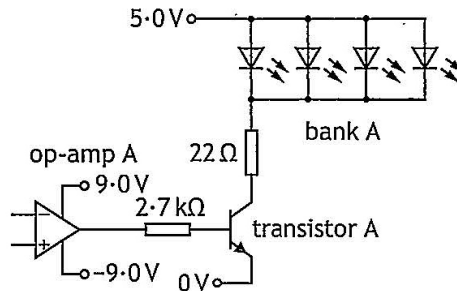

- (b) (i) Calculate the base current for transistor A when op-amp A is saturated positive. (Assume V_{be} is 0.70 V).

3

$$\begin{array}{l}
 V = 0.7 \\
 I = ? \\
 R = 2.7k
 \end{array}
 \left. \vphantom{\begin{array}{l} V \\ I \\ R \end{array}} \right\}
 \begin{array}{l}
 V = IR \\
 I = \frac{V}{R} \\
 I = \frac{0.7}{2.7k} \\
 \underline{\underline{I = 2.59 \times 10^{-4} A}}
 \end{array}$$

Transistor A has a gain (h_{FE}) of 140.


- (ii) Calculate the collector current when op-amp A is saturated.

1

$$\begin{array}{l}
 h_{FE} = 140 \\
 I_c = ? \\
 I_b = 2.59 \times 10^{-4}
 \end{array}
 \left. \vphantom{\begin{array}{l} h_{FE} \\ I_c \\ I_b \end{array}} \right\}
 \begin{array}{l}
 h_{FE} = \frac{I_c}{I_b} \\
 I_c = h_{FE} \times I_b \\
 = 140 \times 2.59 \times 10^{-4} \\
 \underline{\underline{= 0.036 A}}
 \end{array}$$

MARKS
DO NOT
WRITE IN
THIS
MARGIN

8. (continued)

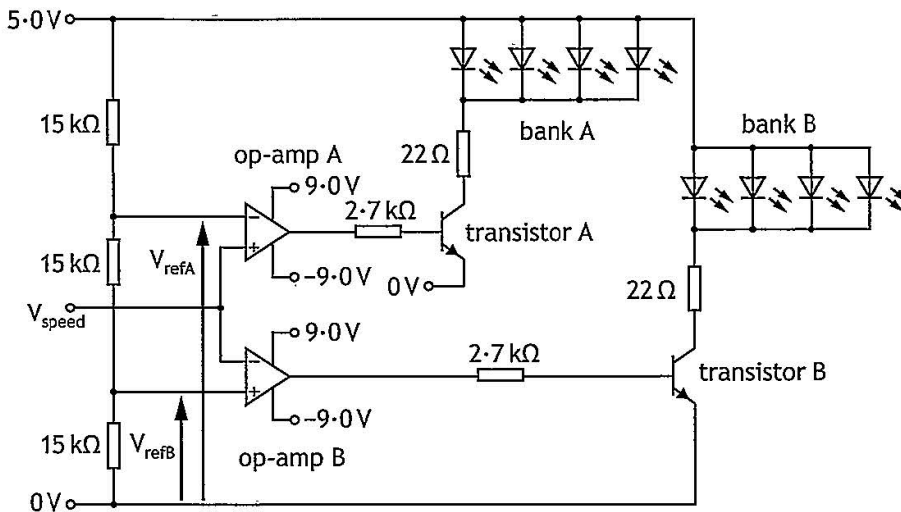

- (c) Describe, with reference to the circuit diagram, what happens to the LEDs as the voltage from the speed sensor (V_{speed}) rises from 0V to 5.0V.

The complete circuit diagram is shown above again for reference.

6

When V_{speed} rises from 0V to 5V
 the voltage is sent to both op-amps
 and because the voltage after to op-amp
 is high enough to saturate both transistors
 both LED banks will turn on but
 Bank B will display telling the user
 to slow down.



* X 8 2 3 7 6 0 1 1 7 *

MARKS

DO NOT
WRITE IN
THIS
MARGIN

8. (continued)

- (d) Describe how the control circuit should be adapted to allow users to change the speeds that switch on the LED banks.


2

the control circuit should have a variable resistor to allow the LED to change when they turn on. Also a high voltage supply.




DO NOT
WRITE IN
THIS
MARGIN

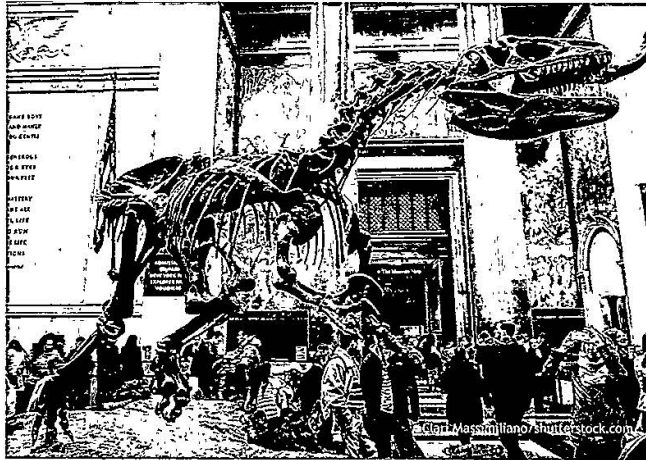9. A team of engineers is asked to design a walkway over a dinosaur exhibit for a natural history museum.



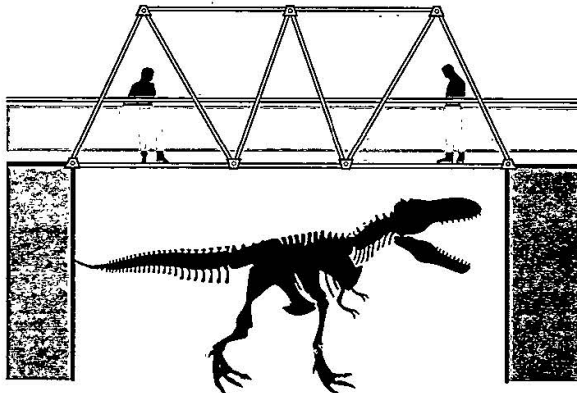
An initial design for a walkway over the top of the exhibit is shown below.



MARKS
DO NOT WRITE IN THIS MARGIN

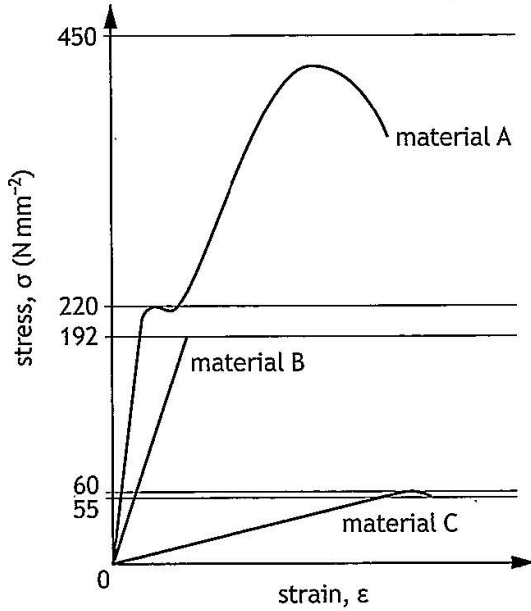9. (continued)

Tensile test results for three materials considered for use in the walkway are shown in the stress-strain graph below.



- (a) (i) Describe, with reference to the stress-strain graph, three different properties of material B in relation to material A or material C.

3

material B is a lot more brittle than material A. Material C can take a lot more strain than material B but not as much stress. Compared to the other two materials, material B is very elastic but brittle at the same time.

- (ii) Identify, with reference to the Data Booklet, material A and material C.

2


Material A mild steel
Material C ABS poly carbonate



MARKS
DO NOT
WRITE IN
THIS
MARGIN

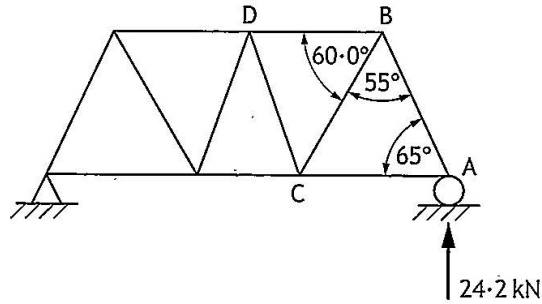9. (continued)

A partially completed free body diagram of the design for the walkway is shown.



- (b) Calculate, using nodal analysis, the magnitude and nature of the forces in members AB, AC, BC and BD.

Complete the table below.

7

Show all working and final units on the page opposite.

Member	Magnitude	Nature
AB	26.2 kN	STRUT
AC	44.76 kN	TIE
BC	-2.9 kN	TIE
BD	41.01 kN	STRUT

9. (b) (continued)

Space for working

$$AO = (-24.2 \sin 55 + 24.2 \cos 55) + (24.2 \sin 65 + 24.2 \cos 65)$$

$$= 26.2 \text{ kN}$$

$$AC = (24.2 \sin 65 - 24.2 \cos 65) + (24.2 \sin 60 + 24.2 \cos 60)$$

$$= 44.76 \text{ kN}$$

$$C = 180 - 120$$

$$= 60^\circ$$

$$BC = (-24.2 \sin 60 + 24.2 \cos 60) + (24.2 \sin 55 - 24.2 \cos 55)$$

$$= -2.9 \text{ kN}$$

$$BD = (24.2 \sin 60 - 24.2 \cos 60) + (-24.2 \sin 65 + 24.2 \cos 65)$$

$$= 41.01 \text{ kN}$$

$$D = 60 + 55$$


$$= 115$$

$$= 180 - 115$$

$$= 65^\circ$$

MARKS
DO NOT
WRITE IN
THIS
MARGIN

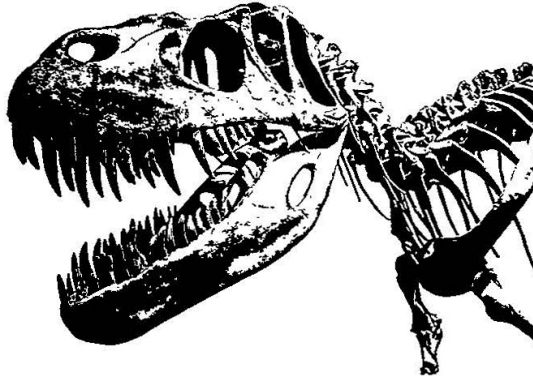10. A mechanical engineer produced a preliminary design for a pneumatic system to open and close a dinosaur skeleton's jaw.



The pneumatic cylinder used to move the jaw has an 8.0 mm diameter aluminium alloy piston rod to support a load of 33.2 kN.

- (a) (i) Calculate the factor of safety applied to the design of the piston rod.

4

$$\begin{aligned}
 \text{F.O.S.} &= \frac{\text{Ultimate stress}}{\text{Safe working stress}} \\
 &= \frac{900}{660.56} \\
 &= \underline{\underline{1.36}}
 \end{aligned}$$

$$\begin{aligned}
 \sigma &= \frac{F}{A} \\
 &= \frac{33.2 \text{ k}}{50.26} \\
 &= 660.56
 \end{aligned}$$

10. (a) (continued)

- (ii) Comment on the appropriateness of the factor of safety of the piston rod.

1

The factor of safety could be higher
but it is fine as it is

The mechanical engineer decides to use a different pneumatic cylinder to support the 33.2 kN load.

The piston rod area is 491 mm² and is made from titanium alloy with a length of 0.78 m.

- (iii) Calculate the change of length in the piston rod under these conditions.

4

$$\left. \begin{aligned} E &= 110 \\ \sigma &= 67.6 \\ e &=? \end{aligned} \right\}$$

$$\begin{aligned} E &= \frac{\sigma}{e} \\ e &= \frac{\sigma}{E} \\ &= \frac{67.6}{110} \\ &= 0.6145 \end{aligned}$$

$$\begin{aligned} \sigma &= \frac{F}{A} \\ &= \frac{33.2 \text{ k}}{491} \\ &= 67.6 \end{aligned}$$

$$\begin{aligned} e &= \frac{\Delta L}{L} \\ \Delta L &= e \times L \\ &= 0.6145 \times 0.78 \\ &= \underline{\underline{0.48 \text{ m}}} \end{aligned}$$


MARKS

DO NOT
WRITE IN
THIS
MARGIN

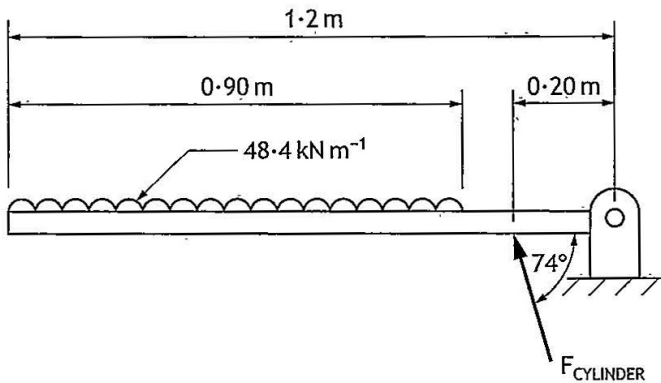10. (continued)

After testing, the pneumatic cylinder is repositioned to move a hinged beam in the jaw of the dinosaur as shown below.

The uniformly distributed load of the jaw is 48.4 kN m^{-1} .



- (b) (i) Calculate the magnitude of force F_{CYLINDER} .

3


$$\begin{aligned}
 F_{\text{cylinder}} \times 74 \times 0.2 &= 43560 \times 1.2 \\
 F_{\text{cylinder}} &= \frac{43560 \times 1.2}{74 \times 0.2} \\
 &= \underline{\underline{3531.8 \text{ N}}}
 \end{aligned}$$

- (ii) Calculate the magnitude and direction of the reaction at the hinge.

4

$$\begin{aligned}
 (3531.8 \sin 74 - 3531.8 \cos 74) + 1.2 \times 43560 &= R \\
 R &= 2421.4 + 52272 \\
 &= \underline{\underline{54693.4 \text{ N}}}
 \end{aligned}$$

11.

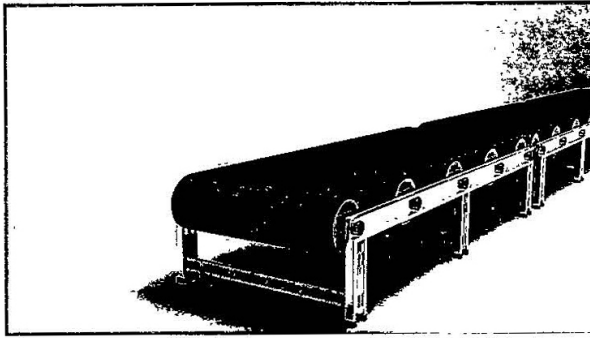

MARKS

DO NOT
WRITE IN
THIS
MARGIN

A proposed design for the operation of a conveyor belt motor has the following specification.

1. The motor will not run if emergency stop(A) is high
2. The motor will run if a pressure sensor(B) is high and a light sensor(C) is low
3. The motor will run if a test switch(D) is high

(a) Complete the Boolean equation for when the motor switches on.

4

$$M = (\bar{A} \cdot B \cdot \bar{C}) + D$$

When the conveyor belt motor starts it uses pulse width modulation to accelerate to a set speed.

The control sequence for the acceleration of the conveyor belt motor has the following steps.


- Initially the MARK = 4 and the SPACE = 2
- Each new pulse increases the MARK by 1
- The acceleration continues until the MARK reaches 20
- The motor turns on
- The motor will then stop when the emergency stop is high or the override switch is low
- A brake engages for 3 seconds
- The sequence repeats

INPUT	PIN	OUTPUT
	7	motor
	6	brake
override switch (released = 0)	1	
emergency stop (pressed = 1)	0	


11. (continued)

(b) Complete, with reference to the specification and input/output table shown opposite, the flowchart for the control of the motor.

13

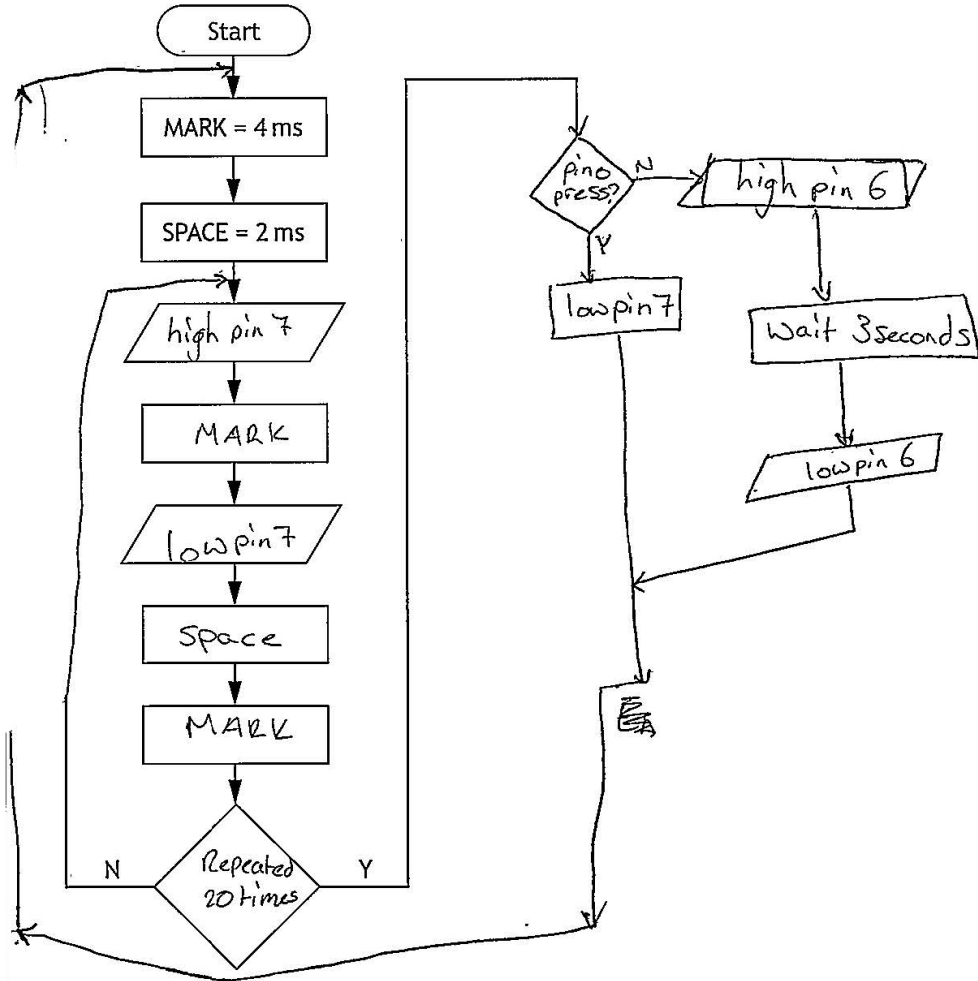

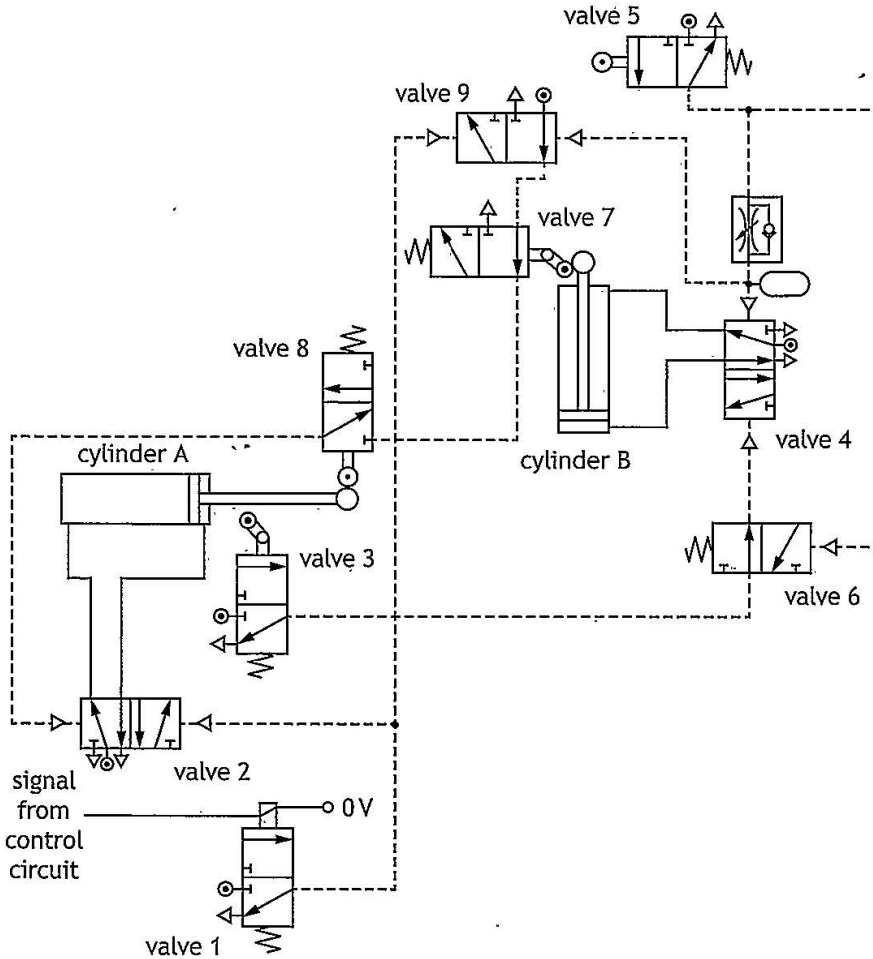12. A pneumatic system will be used in a manufacturing process for holding material in place and then moving it along the production line. The system diagram is shown below.



- (a) Describe, making reference to the diagram above, the operation of the pneumatic circuit.

7

When valve 1 is actuated,

pilot air is sent to valve two which
actuates cylinder A which actuates valve
8 sending pilot air to valve 2 causing
cylinder A to instroke actuating valve

12. (a) (continued)



3 which send ~~3~~ pilot air to valve 6 which continues to valve 4 actuating cylinder B which actuates valve 5 which will send pilot air to valve 6, 4 & 9 where cylinder B will in stroke valve 9 will send pilot air ~~through~~ through valve 7 to valve 8 restarting the process.

[Turn over

DO NOT WRITE IN THIS MARGIN

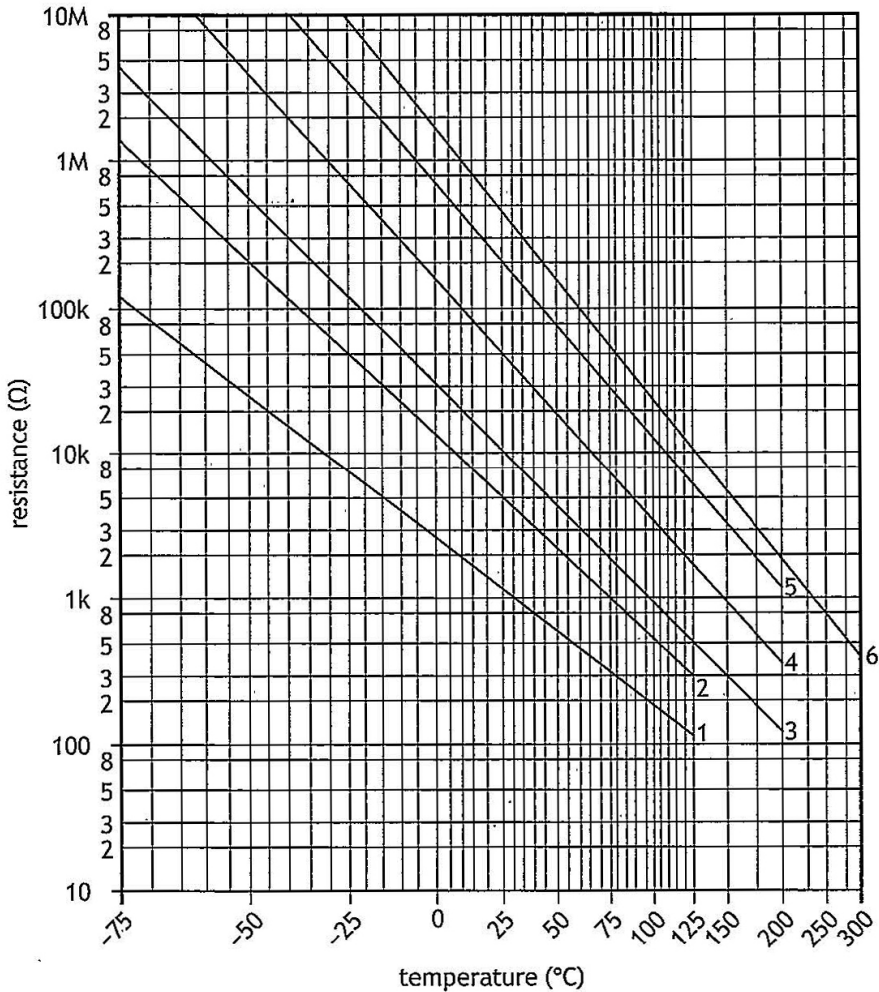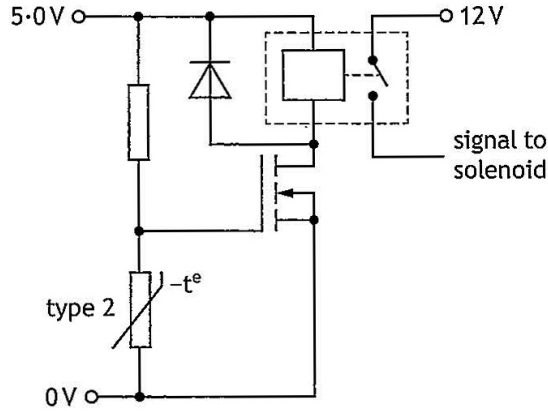12. (continued)

A diagram of the control circuit for the solenoid is shown below. The MOSFET switches on when the gate voltage reaches 3.2V. This happens when the thermistor is at 85 °C.



12. (continued)

MARKS
DO NOT
WRITE IN
THIS
MARGIN

- (b) Calculate, with reference to the graph opposite, the resistance of the fixed resistor to produce a gate voltage of 3.2 V.

3

$$\begin{array}{l}
 V = 5 \\
 I = ? \\
 R = 800
 \end{array}
 \left. \vphantom{\begin{array}{l} V = 5 \\ I = ? \\ R = 800 \end{array}} \right\}
 \begin{array}{l}
 V = IR \\
 I = \frac{V}{R} \\
 = \frac{5}{800} \\
 = 6.25 \times 10^{-3}
 \end{array}
 \begin{array}{l}
 R_{\text{fixed}} = ? \\
 I = 6.25 \times 10^{-3} \\
 V = 3.2 \\
 \\
 V = IR \\
 R = \frac{V}{I} \\
 = \frac{3.2}{6.25 \times 10^{-3}} \\
 = \underline{\underline{512 \Omega}}
 \end{array}$$

The next stage of the manufacturing process requires a drive system.

- (c) Describe one skill and one piece of knowledge a mechanical engineer requires to design the drive system.

2

Skill being able to work with gears
and mechanical systems


Knowledge understanding of a gear
train and what one to use

[Turn over

MARKS
DO NOT
WRITE IN
THIS
MARGIN

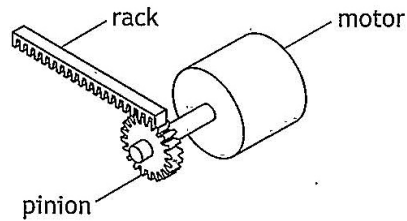12. (continued)

Part of the design involves rotary motion, from a motor, transforming into linear motion.



The pinion gear has 24 teeth and the pitch of the teeth on the rack is 3.0 mm. The rack is required to move 2.75 m in three seconds.


(d) Calculate the required speed of the motor.

3

$$\left. \begin{array}{l} d = 2.75 \\ v = ? \\ t = 3 \end{array} \right\} \quad v = \frac{d}{t} \\ = \frac{2.75}{3} \\ = \underline{\underline{0.91 \text{ m s}^{-1}}}$$

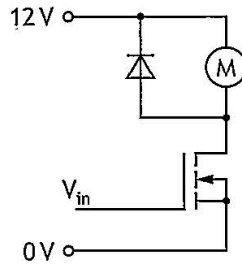12. (continued)

Part of the circuit controlling the motor is shown below.



The motor has a rating of 12 V and 8.5 W.

When the motor is switched on the MOSFET has a resistance of 0.65Ω .

(e) Calculate the MOSFET drain current.

3

$$\begin{array}{l}
 g_m = 8.5 \\
 \Delta V_{gs} = 12 \\
 \Delta I_d = ?
 \end{array}
 \left. \vphantom{\begin{array}{l} g_m = 8.5 \\ \Delta V_{gs} = 12 \\ \Delta I_d = ? \end{array}} \right\}
 \begin{array}{l}
 g_m = \Delta I_d / \Delta V_{gs} \\
 \Delta I_d = g_m / \Delta V_{gs} \\
 = 8.5 / 12 \\
 = \underline{\underline{0.71 A}}
 \end{array}$$

[END OF QUESTION PAPER]